

Dongyun Lee

ID: 112794190

PreLab8: Simple Sequential Circuit

ESE382-L01

Bench #4

```
1  -----
2  --
3  -- Title       : d_structural
4  -- Design      : prelab8
5  -- Author      : Dongyun Lee
6  -- Company     : Stony Brook University
7  --
8  -----
9  --
10 -- File        : X:\ESE382-Lab\Lab8\prelab8\prelab8\src\d_latch.vhd
11 -- Generated   : Mon Mar 25 21:59:07 2024
12 -- From        : interface description file
13 -- By          : Itf2Vhdl ver. 1.22
14 --
15 -----
16 --
17 -- Description :
18 --
19 -----
20
21 ----- d latch -----
22 library ieee;
23 use ieee.std_logic_1164.all;
24
25
26 entity d_latch is
27     port(
28         d : in std_logic;      -- data input
29         le_bar : in std_logic; -- latch enable input
30         ql : out std_logic      -- latch output
31     );
32 end d_latch;
33
34
35 architecture behavioral of d_latch is
36 begin
37     latch: process (d, le_bar)
38     begin
39         if le_bar = '0' then
40             ql <= d; -- updates the output to the value of data(input)
41         end if;
42     end process;
43
44 end behavioral;
45
46 ----- flip flop -----
47 library ieee;
48 use ieee.std_logic_1164.all;
49
50
51
52 entity d_flip_flop is
53     port(
```

```
54         d : in std_logic;
55         clk : in std_logic;
56         qff : out std_logic
57     );
58 end d_flip_flop;
59
60
61 architecture behavioral of d_flip_flop is
62 begin
63     flipflop: process (clk)
64     begin
65         if clk'event and clk = '1' then
66             qff <= d;
67         end if;
68     end process;
69
70 end behavioral;
71
72 ----- top level entity -----
73 library ieee;
74 use ieee.std_logic_1164.all;
75 use work.all;
76
77 entity latch_vs_flip_flop is
78     port (
79         d : in std_logic; -- data input
80         clk : in std_logic; -- clock input
81         ql : out std_logic; -- latch output
82         qff : out std_logic -- flip-flop output
83     );
84 end latch_vs_flip_flop;
85
86 architecture structural of latch_vs_flip_flop is
87 begin
88     u1 : entity d_latch port map (d => d, le_bar => clk, ql => ql);
89     u2 : entity d_flip_flop port map (d => d, clk => clk, qff => qff);
90 end structural;
91
92
93
94
```

```

1  -----
2  --
3  -- Title       : dff_en
4  -- Design      : prelab8
5  -- Author      : Dongyun Lee
6  -- Company     : Stony Brook University
7  --
8  -----
9  --
10 -- File        : X:\ESE382-Lab\Lab8\prelab8\prelab8\src\dff_en.vhd
11 -- Generated   : Tue Mar 26 14:56:15 2024
12 -- From       : interface description file
13 -- By         : Itf2Vhdl ver. 1.22
14 --
15 -----
16 --
17 -- Description :
18 --
19 -----
20 --
21 library ieee;
22 use ieee.std_logic_1164.all;
23
24 entity dff_en is
25     port (
26         d       : in  std_logic;  -- data input
27         clk      : in  std_logic;  -- clock input
28         en       : in  std_logic;  -- enable input
29         rst_bar  : in  std_logic;  -- asynchronous reset
30         q        : out std_logic   -- output
31     );
32 end dff_en;
33
34 architecture behavioral of dff_en is
35 begin
36     flipflop : process (clk, rst_bar)
37     begin
38         if rst_bar = '0' then
39             q <= '0';
40         elsif rising_edge(clk) then
41             if en = '1' then
42                 q <= d;
43             end if;
44         end if;
45     end process;
46 end behavioral;
47
48
49
50

```

```

1  -----
2  --
3  -- Title       : right_shift_reg
4  -- Design      : prelab8
5  -- Author      : Dongyun Lee
6  -- Company     : Stony Brook University
7  --
8  -----
9  --
10 -- File        :
11 X:\ESE382-Lab\Lab8\prelab8\prelab8\src\right_shift_reg.vhd
12 -- Generated   : Tue Mar 26 15:31:56 2024
13 -- From        : interface description file
14 -- By          : Itf2Vhdl ver. 1.22
15 -----
16 --
17 -- Description :
18 --
19 -----
20
21 library ieee;
22 use ieee.std_logic_1164.all;
23
24 entity right_shift_reg is
25     port (
26         d          : in std_logic_vector(3 downto 0); -- parallel input
27         load        : in std_logic;                    -- synchronous load
28         en_shift    : in std_logic;                    -- enable shift if
29         clk         : in std_logic;                    -- clk
30         rst_bar     : in std_logic;                    -- asynchronous reset
31         serial_out  : out std_logic                    -- serial output
32     );
33 end right_shift_reg;
34
35
36 architecture behavior of right_shift_reg is
37     signal memory : std_logic_vector(3 downto 0);
38     begin
39         reg : process (clk, rst_bar)
40         begin
41             if rst_bar = '0' then
42                 memory <= "0000";
43             elsif rising_edge(clk) then
44                 if load = '1' then
45                     memory <= d;
46                 elsif en_shift = '1' then
47                     memory <= memory(3 downto 1) & '0';
48                 end if;
49             end if;
50         end process;
51
52         serial_out <= memory(0);
53

```

```
54 end behavior;  
55
```

```

1  -----
2  --
3  -- Title       : \|3_to_8_decoder\
4  -- Design      : prelab8
5  -- Author      : Dongyun Lee
6  -- Company     : Stony Brook University
7  --
8  -----
9  --
10 -- File        :
11 X:\ESE382-Lab\Lab8\prelab8\prelab8\src\3_to_8_decoder.vhd
12 -- Generated   : Tue Mar 26 16:29:37 2024
13 -- From        : interface description file
14 -- By          : Itf2Vhdl ver. 1.22
15 -----
16 --
17 -- Description :
18 --
19 -----
20 -----input latch -----
21 library ieee;
22 use ieee.std_logic_1164.all;
23
24 entity input_latch is
25     port(
26         a : in std_logic_vector(2 downto 0);
27         le_bar : in std_logic;
28         a_lat : out std_logic_vector(2 downto 0)
29     );
30 end input_latch;
31
32 architecture behavioral of input_latch is
33 begin
34     latch: process (a, le_bar)
35     begin
36         if le_bar = '0' then
37             a_lat <= a; -- updates the output to the value of
38 data(input)
39         end if;
40     end process;
41 end behavioral;
42 -----3 to 8 decoder -----
43 library ieee;
44 use ieee.std_logic_1164.all;
45 use ieee.numeric_std.all;
46
47 entity decoder_3to8 is
48     port(
49         a_lat : in std_logic_vector(2 downto 0);
50         g : in std_logic;
51         y : out std_logic_vector(0 to 7)
52     );
53 end decoder_3to8;
54
55 architecture cond of decoder_3to8 is

```

```

56 begin
57     decoder : process (a_lat, g)
58     begin
59         y <= "00000000";
60         if g = '1' then
61             for i in 0 to 7 loop
62                 if unsigned(a_lat) = to_unsigned(i,3) then
63                     y(i) <= '1';
64                 end if;
65             end loop;
66         end if;
67     end process;
68 end cond;
69
70
71 -----top level entity latched 3 to 8 decoder -----
72 library ieee;
73 use ieee.std_logic_1164.all;
74 use ieee.numeric_std.all;
75 use work.all;
76
77 entity latched_3to8_decoder is
78     port(
79         a : in std_logic_vector(2 downto 0);
80         le_bar, e1_bar, e2 : in std_logic;
81         y : out std_logic_vector(0 to 7)
82     );
83 end latched_3to8_decoder;
84
85 architecture structural of latched_3to8_decoder is
86     signal a_lat : std_logic_vector(2 downto 0);
87     signal g : std_logic;
88     begin
89         u0 : entity input_latch port map (a => a, le_bar => le_bar, a_lat =>
a_lat);
90         u1 : entity decoder_3to8 port map (a_lat => a_lat, g => g, y => y);
91
92         u2 : g <= '1' when (e1_bar = '0') and (e2 = '1') else '0';
93     end structural;
94

```



```

1  -----
2  --
3  -- Title       : latched_3to8_decoder_tb
4  -- Design      : prelab8
5  -- Author      : Dongyun Lee
6  -- Company     : Stony Brook University
7  --
8  -----
9  --
10 -- File        : Z:\Desktop\SBU 2024 Spring\ESE
    382\lab-backup\Lab8\prelab8\prelab8\src\latched_3to8_decoder_tb.vhd
11 -- Generated   : Sat Mar 30 16:39:02 2024
12 -- From        : interface description file
13 -- By          : Itf2Vhdl ver. 1.22
14 --
15 -----
16 --
17 -- Description : testbench for latched 3 to 8 decoder
18 --
19 -----
20 --
21 library ieee;
22 use ieee.std_logic_1164.all;
23 use ieee.numeric_std.all;
24 use work.all;
25
26 entity latched_3to8_decoder_tb is
27 end latched_3to8_decoder_tb;
28
29
30 architecture latched_3to8_decoder_tb of latched_3to8_decoder_tb is
31     signal a      : std_logic_vector(2 downto 0);
32     signal le_bar : std_logic;
33     signal e1_bar : std_logic;
34     signal e2      : std_logic;
35     signal y       : std_logic_vector(0 to 7);
36
37 type test_vector is record
38     le_bar : std_logic;
39     e1_bar : std_logic;
40     e2      : std_logic;
41     a       : std_logic_vector(2 downto 0);
42     y       : std_logic_vector(0 to 7);
43 end record;
44
45 type test_vectors is array (natural range <>) of test_vector;
46
47 constant test_table : test_vectors := (
48     -- e1_bar e1_bar e2      a       y
49     ( '1', '1', '1', "1", "00000000"), -- When E1 is low, all outputs are
    low
50     ( '1', '1', '0', "1", "00000000"), -- When E2 is low, all outputs are
    low

```


```

51      -- Latch enabled and E1 is low, decoder is active
52      ( '0', '0', '1', "000", "10000000"), -- Input A is 0, Y0 is high
53      ( '0', '0', '1', "001", "01000000"), -- Input A is 1, Y1 is high
54      ( '0', '0', '1', "010", "00100000"), -- Input A is 2, Y2 is high
55      ( '0', '0', '1', "011", "00010000"), -- Input A is 3, Y3 is high
56      ( '1', '0', '1', "---", "-----"), -- When LE is high, outputs
are stable
57      ( '0', '0', '1', "100", "00001000"), -- Input A is 4, Y4 is high
58      ( '0', '0', '1', "101", "00000100"), -- Input A is 5, Y5 is high
59      ( '0', '0', '1', "110", "00000010"), -- Input A is 6, Y6 is high
60      ( '0', '0', '1', "111", "00000001") -- Input A is 7, Y7 is high
61 );
62
63 begin
64     UUT : entity latched_3to8_decoder port map (
65         a => a,
66         le_bar => le_bar,
67         e1_bar => e1_bar,
68         e2 => e2,
69         y => y
70     );
71     tb : process
72     variable memory : std_logic_vector(7 downto 0);
73     begin
74
75         for i in test_table'range loop
76             a <= test_table(i).a;
77             le_bar <= test_table(i).le_bar;
78             e1_bar <= test_table(i).e1_bar;
79             e2 <= test_table(i).e2;
80             wait for 20ns;
81             if le_bar = '1' and e1_bar = '0' and e2 = '1' then
82                 assert y = memory;
83                 report "Error at le_bar = '1' and e1_bar = '0' and e2 =
'1'. Output should be stable"
84                     severity error;
85             else
86                 memory := test_table(i).y;
87                 assert y = test_table(i).y
88                 report "Error at input a, le_bar, e1_bar, e2 : " &
to_string(a) & to_string(le_bar) & to_string(e1_bar) & to_string(e2)
89                     severity error;
90             end if;
91
92         end loop;
93         std.env.finish;
94     end process;
95
96
97
98 end latched_3to8_decoder_tb;
99

```


## Design task 1

### D-flip-flop waveform

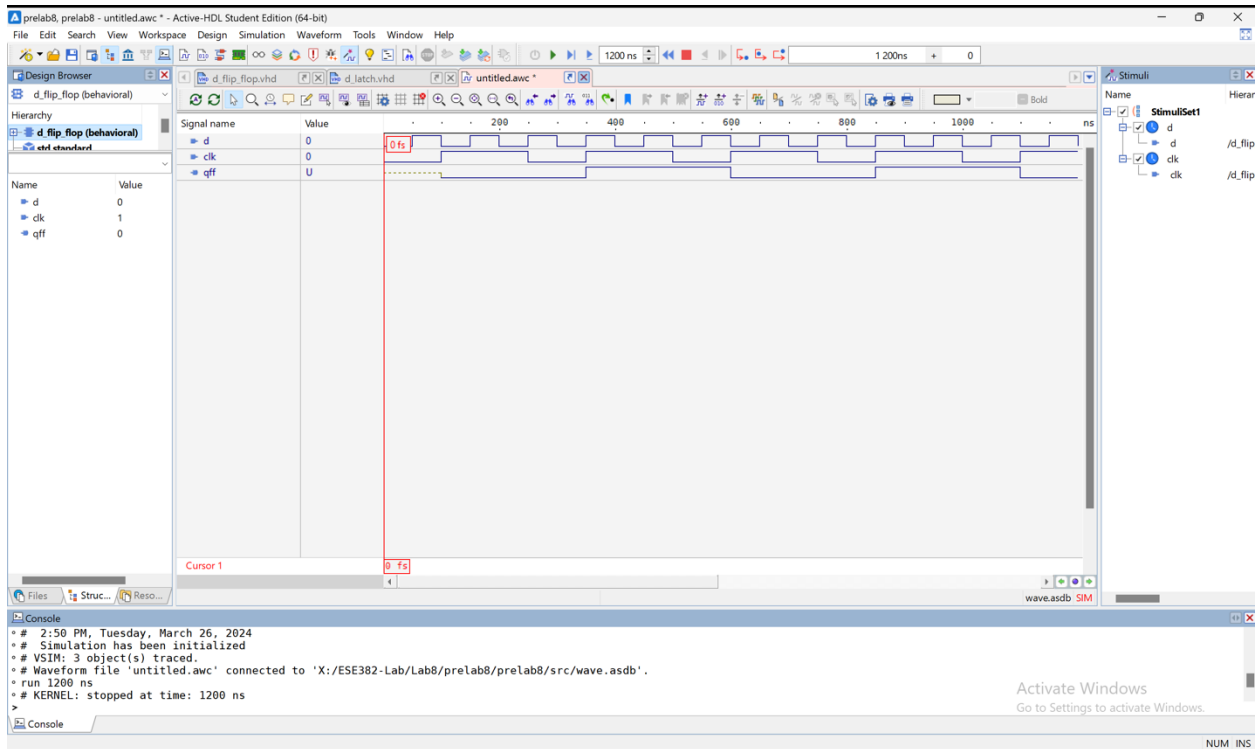


Qff copy d at rising clock edge.

## D-latch waveform

 


Ql copy d when le\_bar = '0'.

## Latch vs. flipflop waveform

 


Qff copy d when rising clock edge and ql copy d when clock = '0'.

Sketch of the verification waveform

 


## Design task 2

### waveform

 


When en = '1' and rst\_bar = '1' q copy d when rising clock edge.

Sketch of the verification waveform

 

## Design task 3


### Waveform

 

Rst\_bar is the only asynchronous input. When rst\_bar = '0' all the bits of the shift register are 0s. The output loads four bits of input on a rising clock edge when load = '1'.

## Design task4

## Waveform

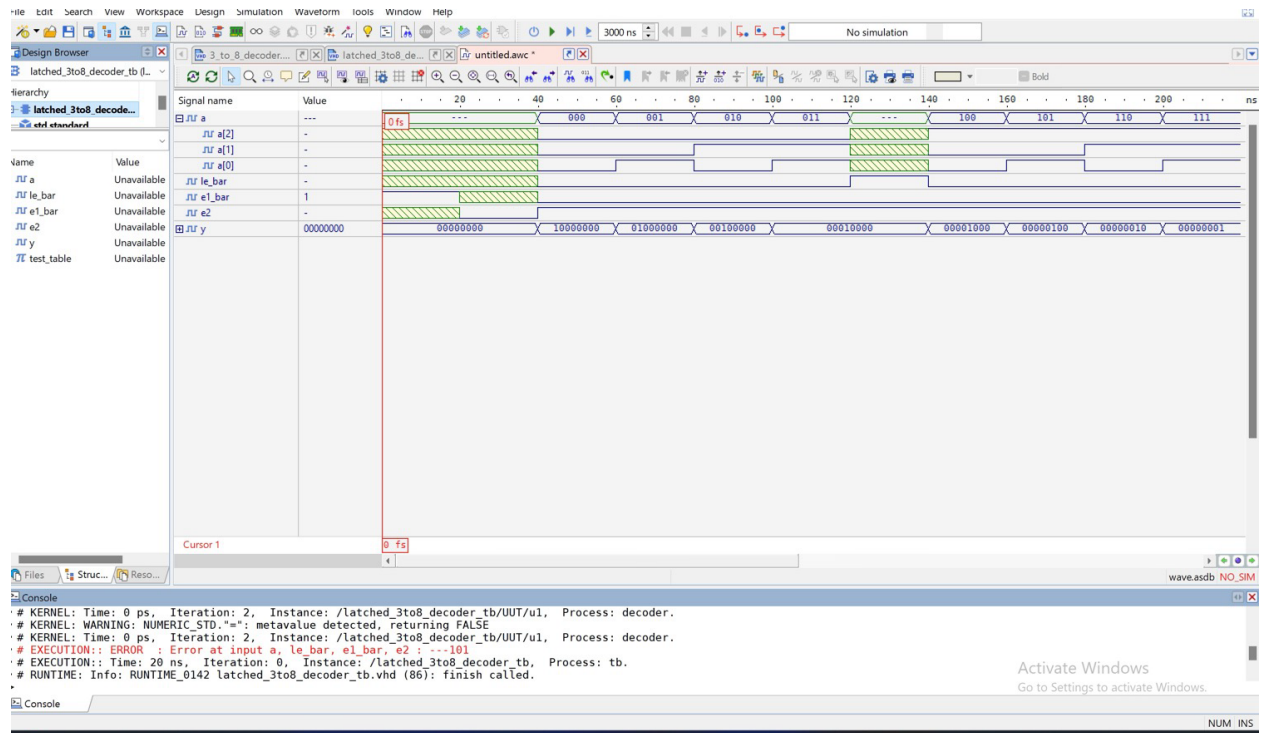

When either  $e1\_bar = '1'$  and  $e2 = '0'$ , the output must be all 0s. When  $le\_bar = '0'$   $e1\_bar = '0'$  and  $e2 = '1'$  then the output  $y$  is as expected on the truth table. When  $le\_bar = '1'$ , the output stays the same (as it is shown for  $y = "00010000"$ ).